
 


# ECE 622 Lab 1

Written by: Shu-Lin Shih, Jaideep


## A.1

ex1: use the following method to draw ex1 transition state graph

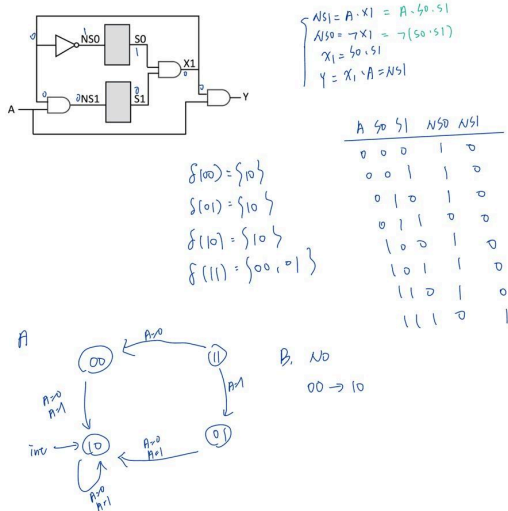

**stoplight1:** write a testbench for stoplight module, used to test all state transitions and display the results based on changes in ped


S=0000	Ped=0 -> 0001	Ped=1 -> 0001
S=0001	Ped=0 -> 0010	Ped=1 -> 0010
S=0010	Ped=0 -> 0011	Ped=1 -> 0011
S=0011	Ped=0 -> 0100	Ped=1 -> 0110
S=0100	Ped=0 -> 0101	Ped=1 -> 0111
S=0101	Ped=0 -> 0101	Ped=1 -> 1000
S=0110	Ped=0 -> 0111	Ped=1 -> 0111
S=0111	Ped=0 -> 1000	Ped=1 -> 1000
S=1000	Ped=0 -> 1001	Ped=1 -> 1001
S=1001	Ped=0 -> 0000	Ped=1 -> 0000
S=1010	Ped=0 -> 1011	Ped=1 -> 1011
S=1011	Ped=0 -> 0000	Ped=1 -> 0010
S=1100	Ped=0 -> 1001	Ped=1 -> 1011
S=1101	Ped=0 -> 0000	Ped=1 -> 0000
S=1110	Ped=0 -> 1011	Ped=1 -> 1011
S=1111	Ped=0 -> 0000	Ped=1 -> 0000

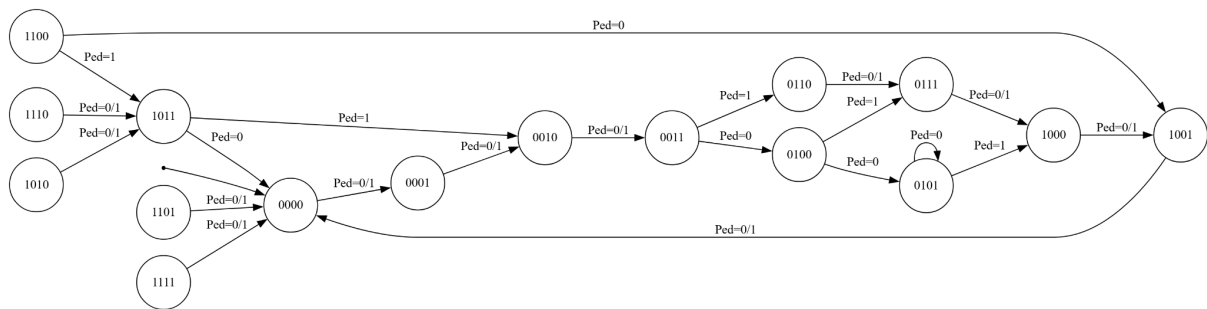
 
## A.2

ex1: according to transition state graph 00 will never reach target state 11

stoplight1: 0000(ped=0/1)->0001(ped=0/1)->0010(ped=0/1)->0011(ped=0)->0100



## A.3 (not sure : should we add initial state?)

ex1:


A	B
1	1
2	1
3	1
4	1
5	1
6	1
7	1
8	1
9	1
10	1
11	1
12	1
13	1
14	1
15	1
16	1
17	1
18	1
19	1
20	1

stoplight1:

1	1
2	2
3	3
4	5
5	7
6	8
7	9
8	9
9	9
10	9
11	9
12	9
13	9
14	9
15	9
16	9
17	9
18	9
19	9
20	9

 
# A.4

ex1: initial state will never reach target state




```
ex1: Target state 11 NOT reached within 100000 cycles (TIMED OUT)
$finish called at time : 1000006 ns : File "C:/Users/maxf2/Desktop/embedded system/lab1_files/tb_ex1.v" Line 51
```

 ex2: initial state will never reach target state




```
# run 1000ns
INFO: [USF-XSim-96] XSim completed. Design snapshot 'tb_ex2_behav' loaded.
INFO: [USF-XSim-97] XSim simulation ran for 1000ns
launch_simulation: Time (s): cpu = 00:00:03 ; elapsed = 00:00:10 . Memory (MB): peak = 21
run -all
ex2: Target state 111111111111 NOT reached within 100000 cycles (TIMED OUT)
```

stoplight1:

 

```
INFO: [USF-XSim-97] XSim simulation ran for 1000ns
launch_simulation: Time (s): cpu = 00:00:03 ; elapsed = 00:00:10 . Memory (MB): peak = 2562.023 ; gain = 0.000
ERROR: [Common 17-180] Spawn failed: No error
run -all
stoplight1: Target state 0100 REACHED at cycle 52
$finish called at time : 516 ns : File "C:/Users/maxf2/Desktop/embedded system/lab1_files/tb_soptlight1.v" Line 39
```

stoplight2:

 

```
INFO: [USF-XSim-96] XSim completed. Design snapshot 'tb_stoplight2_behav' loaded.
INFO: [USF-XSim-97] XSim simulation ran for 1000ns
) launch_simulation: Time (s): cpu = 00:00:12 ; elapsed = 00:00:11 . Memory (MB): peak = 2658.184 ; gain = 0.000
) run -all
stoplight2: Target state 01000 REACHED at cycle 1357
) $finish called at time : 13585 ns : File "C:/Users/maxf2/Desktop/embedded system/lab1 files/tb stoplight2.v" Line 41
```

## stoplight1 testbench

```
1 `timescale 1ns/1ps
2
3 module tb_stoplight1;
4     reg clock, Ped;
5     wire SigG, SigY, SigR;
6     integer i;
7     integer reached;
8
9     spotlight1 spotlight1 (
10         .clock(clock),
11         .Ped(Ped),
12         .SigG(SigG),
13         .SigY(SigY),
14         .SigR(SigR)
15     );
16
17     initial clock = 0;
18     always #5 clock = ~clock;
19
20     initial begin
21         reached = 0;
22         Ped = 0;
23         spotlight1.S3 = 0;
24         spotlight1.S2 = 0;
25         spotlight1.S1 = 0;
26         spotlight1.S0 = 0;
27
28         for (i = 1; i <= 100000; i = i + 1) begin
29             Ped = $random % 2;
30             @(posedge clock);
31
32             // Target:0100
33             if (spotlight1.S3 == 0 && spotlight1.S2 == 1 && spotlight1.S1 == 0 && spotlight1.S0 == 0) begin
34                 $display("stoplight1: Target state 0100 REACHED at cycle %0d", i);
35                 reached = 1;
36                 @(posedge clock);
37                 @(posedge clock);
38                 $finish;
39             end
40         end
41
42         if (reached == 0)
43             $display("stoplight1: Target state 0100 NOT reached within 100000 cycles (TIMED OUT)");
44
45         $finish;
46     end
47
48 endmodule
```

## A.5

The result for stoplight1 is consistent with the result from A.2. We know that stoplight1 will reach the target state 0100 in A.2 and A.4 simulation shows the same result.

# C

ex1:

1		1
2		1
3		1
4		1
5		1
6		1
7		1
8		1
9		1
10		1
11		1
12		1
13		1
14		1
15		1
16		1
17		1
18		1
19		1
20		1

ex5:

1		8
2		14
3		18
4		22
5		26
6		28
7		28
8		28
9		28
10		28
11		28
12		28
13		28
14		28
15		28
16		28
17		28
18		28
19		28
20		28